



Experiment No. 3

Implement code conversion

Name: OM PATIL

Roll Number: 43

Date of Performance:

Date of Submission:

Aim - TO realize half adder and full adder.

Objective -

- 1) The objective of this experiment is to understand the function of Half-adder, Full-adder, Half-subtractor and Full-subtractor.
- 2) Understand how to implement Adder and Subtractor using logic gates.

Components required -

1. IC's - 7486(X-OR), 7432(OR), 7408(AND), 7404 (NOT)
2. Bread Board
3. Connecting wires.

Theory -

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary numbers A and B. It is the basic building block for addition of two single bit numbers. This circuit has two outputs CARRY and SUM.

$$\begin{aligned}\text{Sum} &= A \oplus B \\ \text{Carry} &= A \cdot B\end{aligned}$$

Full adder is a combinational logic circuit with three inputs and two outputs. Full adder is developed to overcome the drawback of HALF ADDER circuit. It can add two one bit numbers A and B. The full adder has three inputs A, B, and CARRY in, the circuit has two outputs CARRY out and SUM.

$$\text{Sum} = (A \oplus B) \oplus C_{in}$$

Caro, -  $AB + C_{in}$  (AOB)

Subtracting a single-bit binary value B from another A (i.e.  $A - B$ ) produces a difference bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the halfSubtractor are

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A' B$$



**Vidyavardhini's College of Engineering & Technology**


**Department of Artificial Intelligence and Data Science**

difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are

$$\text{Difference} = (A \oplus B) \oplus C_{in}$$


$$\text{Borrow} = A'B + A'(C_{in}) + B(C_{in})$$

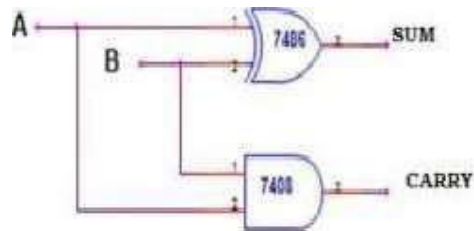Circuit Diagram and Truth Table Half-adder



A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


## Full-adder

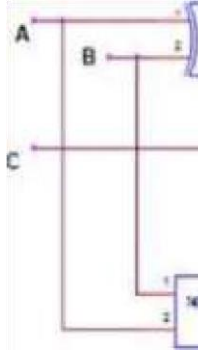

A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Vidyavardhini's College of Engineering & Technology  
Department of Artificial Intelligence and Data Science

Screen Short:

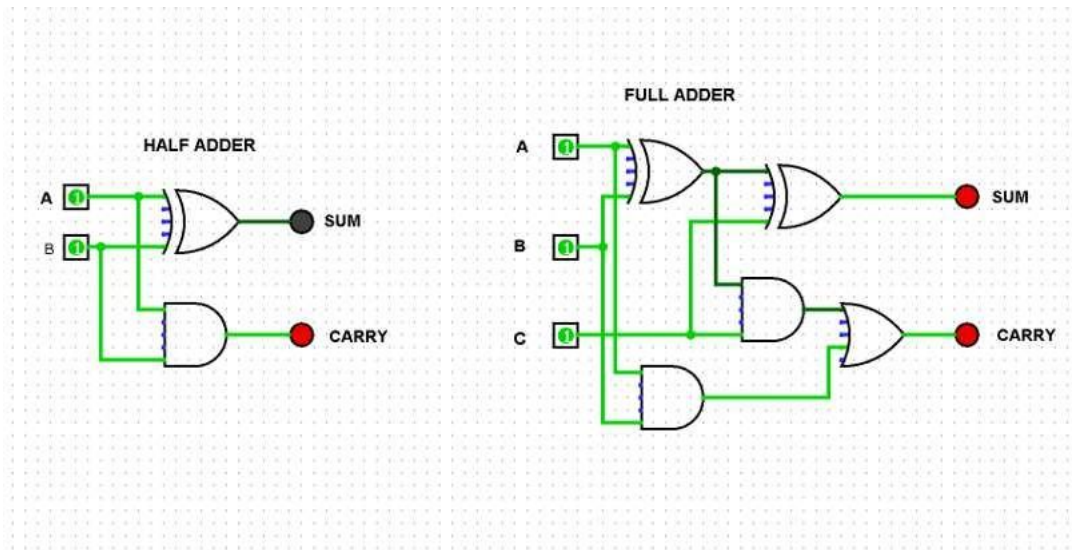

Procedure I.

Verify the gates. 2. Make the connections as per the circuit diagram.

3. Switch on VCC and apply various combinations of input according to truth table. 4. Note down the output readings for half/full adder and half/full subtractor, Sum/difference and the carry/borrow bit for different combinations of inputs verify their truth tables.

Conclusion –

The experiment showcased building a half adder and a full adder, demonstrating the basics of binary addition in digital circuits. The half adder adds two binary digits, while the full adder extends this to three inputs, setting the foundation for arithmetic operations and complex computational processes in digital logic design.